CIRCUIT:

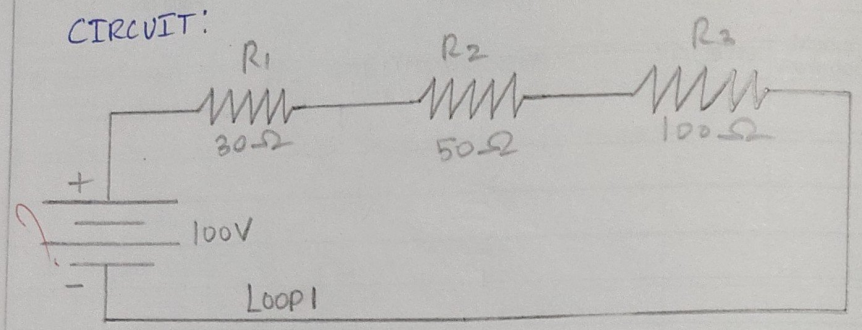

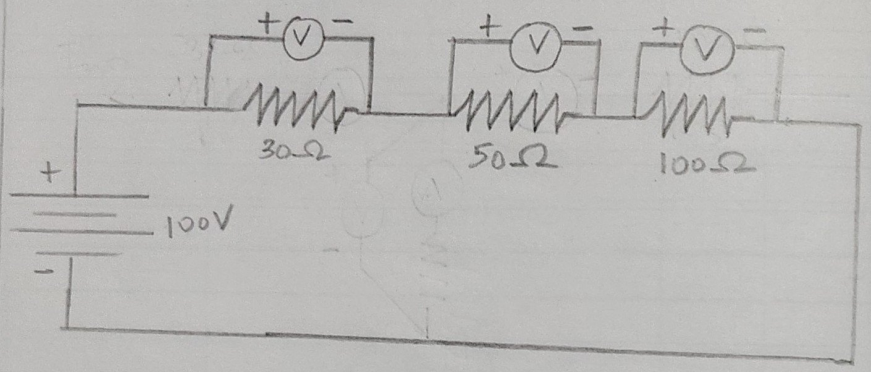

TABULATION:

KVL	Source (V)	$V_{30\Omega}$ (V)	$V_{50\Omega}$ (V)	$V_{100\Omega}$ (V)	$V_{30\Omega}+V_{50\Omega}+V_{100\Omega}$ (V)
Theory	100	16.68V	27.8V	55.6V	100.05
Practical	100	16.7V	27.8V	55.6V	100.1

Expt. No. 1

Page No. 2

16.2.26 1. VERIFICATION OF KIRCHOFF'S VOLTAGE LAW AND KIRCHOFF'S CURRENT LAW

AIM:

To verify Kirchoff's voltage law for 1 and Kirchoff's current law in node A for the following circuit

APPARATUS REQUIRED:

Laptop with Proteus software.

THEORY:

According to Kirchoff's voltage law sum of potential raises are equal to sum of potential drop in a loop.

In loop 1 By KVL:

$$V = V_1 + V_2 + V_3 \longrightarrow (1)$$

$$100 = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 30 + 50 + 100$$

$$R_{eq} = 180\ \Omega$$

$$I = \frac{V}{R_{eq}} = \frac{100}{180} = 0.556\ A$$

$$V_1 = V_{30\Omega} = IR_1 = 0.556 \times 30 = 16.68\ V$$

$$V_2 = V_{50\Omega} = IR_2 = 0.556 \times 50 = 27.8\ V$$

$$V_3 = V_{100\Omega} = IR_3 = 0.556 \times 100 = 55.6\ V$$

CIRCUIT:

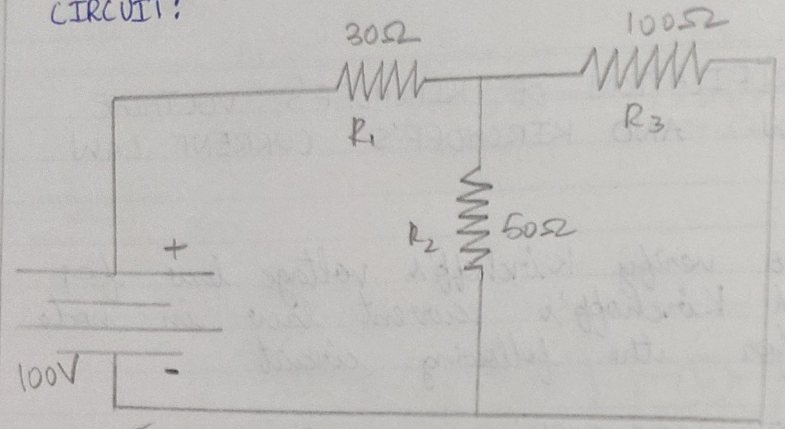

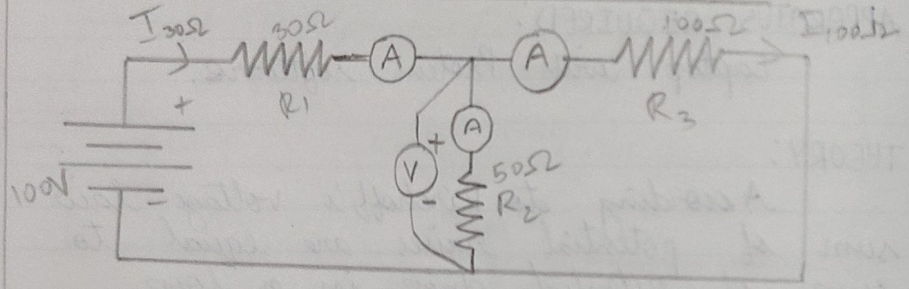

TABULATION:

KCL	$I_{30\Omega}$	$I_{50\Omega}$	$I_{100\Omega}$	V_A
Theory	-1.48A	1.85A	0.56A	52.63.V
Practical	1.58A	1.05A	0.53A	52.6V

Substitute V_1, V_2 and V_3 values in ①,

$100 = 16.68 + 27.8 + 55.6$

$100V = 100V$

Hence proved.

KIRCHOFF'S CURRENT LAW:

In a junction, incoming current is equal to outgoing current.

At node A,

$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0.$

$$\frac{V-100}{30} + \frac{V}{50} + \frac{V}{100} = 0.$$

$$V\left[\frac{1}{30} + \frac{1}{50} + \frac{1}{100}\right] - \frac{100}{30} = 0$$

$$V(0.0633) - 3.333 = 0.$$

$$V = \frac{3.333}{0.0633}$$

$$V = 52.63V$$

$$I_{30\Omega} = \frac{V-100}{30} = \frac{52.63-100}{30} = -1.58A$$

$$I_{50\Omega} = \frac{V}{50} = \frac{52.63}{50} = 1.05A$$

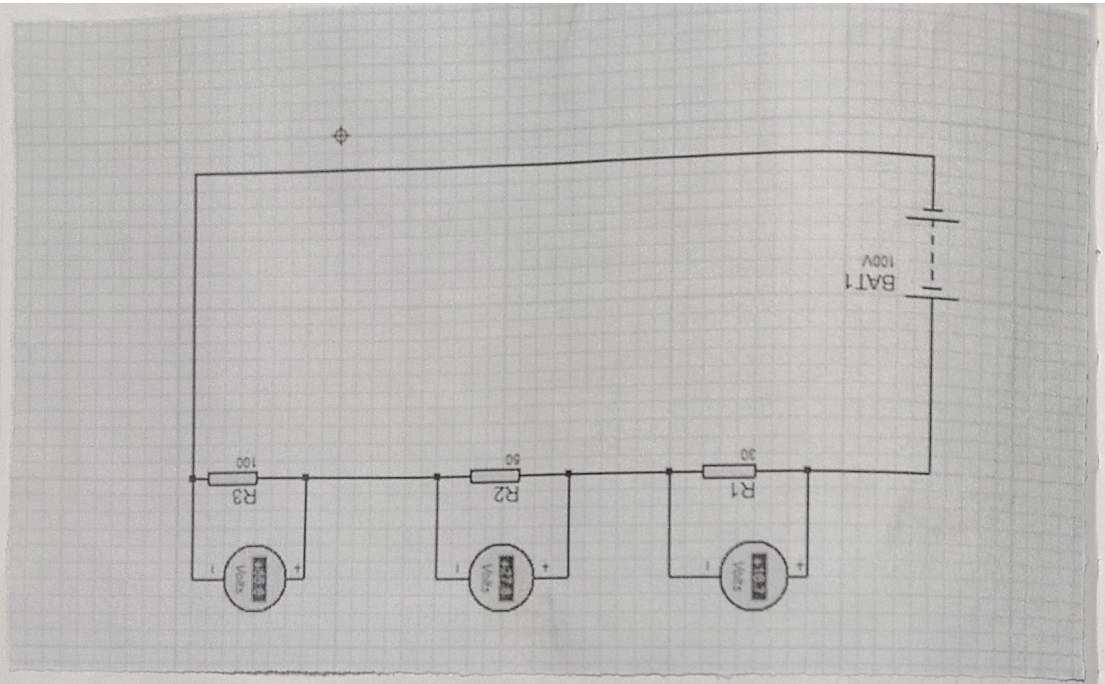

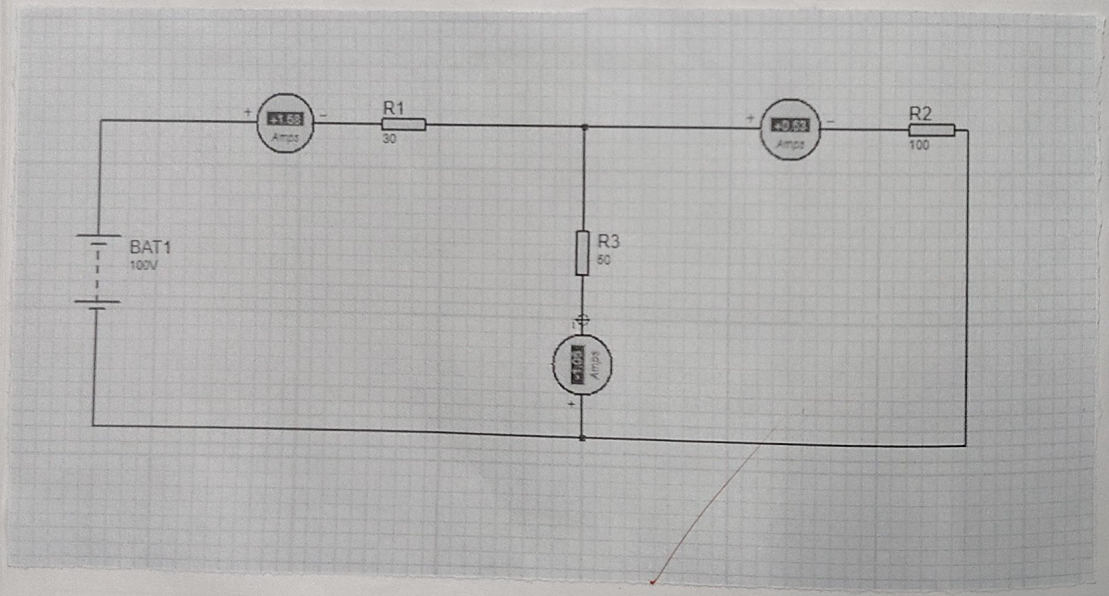

$$I_{100\Omega} = \frac{V}{100} = \frac{52.63}{100}$$

$$= 0.53A$$

At node A,

$$I_{30\Omega} + I_{50\Omega} + I_{100\Omega} = 0$$

$$-1.58 + 1.05 + 0.58 = 0$$

Hence proved.

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST

99

18/03/26

RESULT:

Thus, the Kirchoff's voltage law and Kirchoff's current law has been verified successfully.